
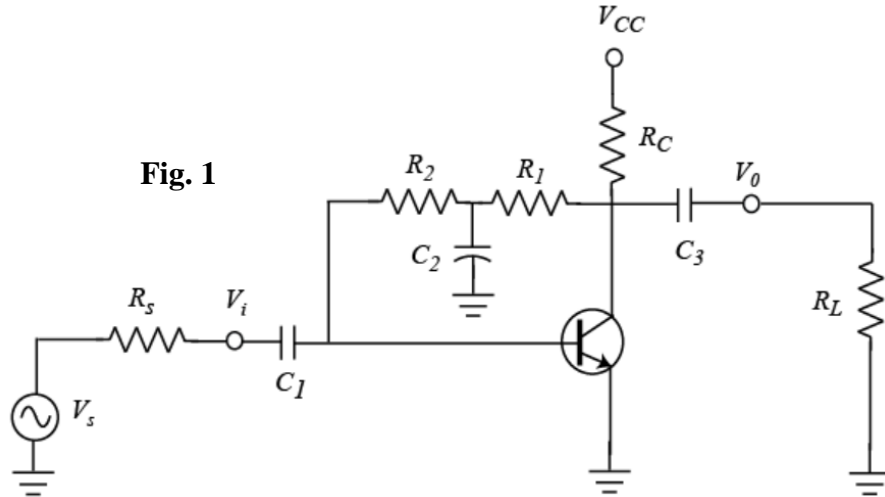


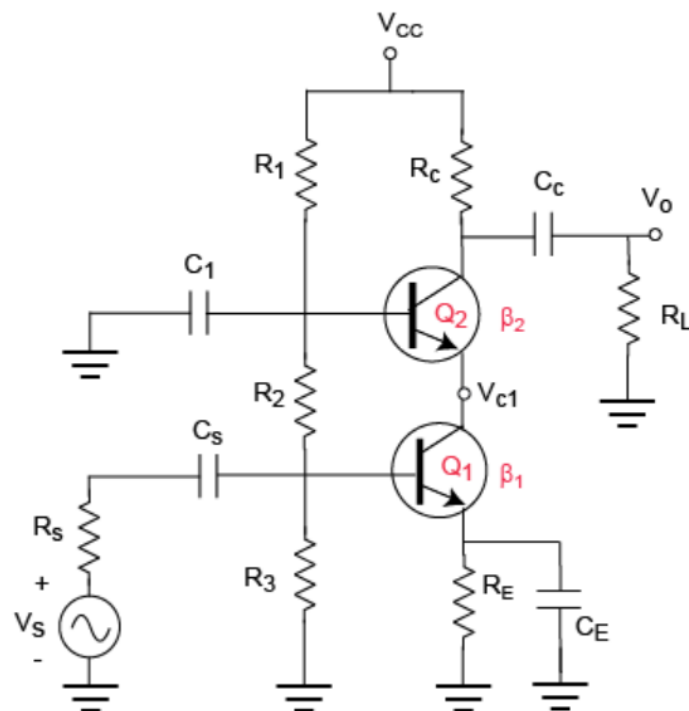
1. For the network of Fig. 1, assume $V_{cc} = 15\text{ V}$, $R_C = 4\text{ k}\Omega$, $R_I = 80\text{ k}\Omega$, $R_2 = 130\text{ k}\Omega$, $R_S = 0.3\text{ k}\Omega$, $R_L = 7\text{ k}\Omega$, $C_1 = 20\text{ }\mu\text{F}$, $C_2 = 0.02\text{ }\mu\text{F}$, $C_3 = 20\text{ }\mu\text{F}$, $V_s = 15\text{ mV}$, $\beta = 150$, $r_o = 40\text{ k}\Omega$. Determine:
 (a) I_B , I_E , (b) Z_i , (c) Z_o , (d) A_{V_s} and (e) V_o (30 pt)



2. Consider a BJT cascade amplifier shown in Figure 2. Assume $V_{cc} = 20\text{ V}$, $R_C = 2\text{ k}\Omega$, $R_I = 4.7\text{ k}\Omega$, $R_2 = 5.6\text{ k}\Omega$, $R_3 = 4.7\text{ k}\Omega$, $R_S = 0.2\text{ k}\Omega$, $R_E = 1.3\text{ k}\Omega$, $R_L = 6.8\text{ k}\Omega$, $C_c = 20\text{ }\mu\text{F}$, $C_E = 30\text{ }\mu\text{F}$, $C_1 = 10\text{ }\mu\text{F}$, $C_s = 5\text{ }\mu\text{F}$, $V_s = 12\text{ mV}$, $\beta_1 = \beta_2 = 180$, $r_o = 60\text{ k}\Omega$. Determine: (a) I_{B1} , V_{B2} , I_{C2} , (b) V_{C1} , (c) A_{V2} and A_{V1} (d) V_o (30 pt)



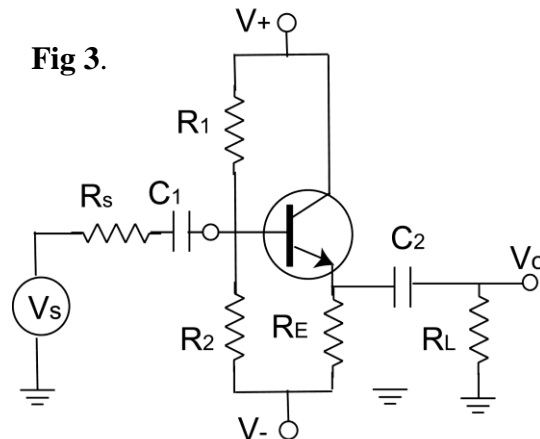3. Consider the circuit shown in Fig 3. The transistor parameters are $\beta = 180$ and $V_A = \infty$. $V_+ = +9\text{ V}$, $V_- = -9\text{ V}$, $R_1 = 10\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $R_E = 500\text{ }\Omega$, $R_L = 300\text{ }\Omega$, $R_s = 1\text{ k}\Omega$, $V_{BE(on)} = 0.7\text{ V}$. Assume C_1, C_2 and C_3 act as short for AC. Find (a) I_C (b) V_{CE} (c) Plot DC load line and mark Q point (d) Calculate the small-signal voltage gain V_o/V_s . (e) Determine the output resistance Z_o (20pt)



4. Consider the circuit shown in Fig 2. Use LT-SPICE to perform AC analysis. Draw V_o as a function of input frequency f for $f = 10\text{ Hz}$ to 1 MHz . Note $V_s = 0.012\sin(\omega t)$. Answer all questions in Problem 2. Send your LT-SPICE file to NTHU-E-Learner system before the deadline (5/20/2020, 23:30 pm). (20 pt)

Note:

- (1) BJT NPN : 2N3904 (You can pickup other BJT if you cannot find this model in your device library.)
- (2) Use your student ID as the file name e.g. 101123456.asc
- (2) Use the “TEXT” function (Edit \rightarrow text) to write down your answers and attach them on the worksheet.