

# National Tsing Hua University

## Department of Physics

PHYS3090

Applied Electronics I

108 Spring

Final Exam

注意：每個答案皆要有嚴謹的推導過程或詳細的推論理由。考題總分為 121 分。

1. (15 points) In Figure 1,  $R_1 = 240\text{k}\Omega$ ,  $R_2 = 160\text{k}\Omega$ ,  $R_C = 3.2\text{k}\Omega$ ,  $R_{E1} = 100\Omega$ ,  $R_{E2} = 1.5\text{k}\Omega$ , and  $V_{CC} = 20\text{V}$ . The transistor in the active region has  $\beta_{DC} = \beta_{ac} = 100$ ,  $V_{BE} \approx 1.0\text{V}$ , and negligible  $r_e'$ . When  $V_s = 0$ , what are  $V_B$  (the voltage at the base),  $I_C$  (current flowing into the collector) and  $V_{CE}$  (the collector-emitter voltage)?
2. (20 points) Follow problem 1. (a) Please find the input and output impedances of the circuit (excluding  $V_s$  and  $R_L$ ). (b) When  $V_s = 20 \sin(\omega t)$  mV and  $R_L = 320\text{k}\Omega$ , what is  $V_L$  (voltage across  $R_L$ )? (c) When  $V_s = 10 \sin(\omega t)$  mV and  $R_L = 3.2\text{k}\Omega$ , what is  $V_L$ ?
3. (20 points) In Figure 2,  $R_1 = 12\text{k}\Omega$ ,  $R_2 = 8\text{k}\Omega$ ,  $R_E = 200\Omega$ , and  $V_{CC} = 20\text{V}$ . The two transistors are the same and, in the active region, they have  $\beta_{DC} = \beta_{ac} = 30$ ,  $V_{BE} \approx 1.0\text{V}$ , and negligible  $r_e'$ . (a) When  $V_{in} = 0$ , what are  $V_{B1}$  (the voltage at the base of  $Q_1$ ),  $I_E$  (current flowing through  $R_E$ ), and  $V_{CE2}$  (the collector-emitter voltage of  $Q_2$ )? (b) When  $V_{in} = 5 \sin(\omega t)$  V, what is  $I_{b1}$  (ac current flowing into the base of  $Q_1$ )?
4. (20 points) In Figure 3,  $R_1 = 2\text{k}\Omega$ ,  $R_2 = 2\text{k}\Omega$ ,  $R_L = 8\Omega$ , and  $\pm V_{CC} = \pm 15\text{V}$ . The two transistors  $Q_1$  and  $Q_2$  all have  $\beta_{DC} = \beta_{ac} = 40$ ,  $V_{BE} \approx 1.0\text{V}$ , and  $r_e' = 2\Omega$ . The input signal is  $V_s = 12 \sin(\omega t)$  V. What are the average power consumptions of  $Q_1$ ,  $R_L$ , the entire amplifier (including  $R_L$  and excluding  $\pm V_{CC}$ )? What is the average power provided by  $V_s$ ?
5. (10 points) An audio amplifier has input and output impedances of  $10\text{k}\Omega$  and  $50\Omega$ , and a voltage gain of 1,500. The amplifier's input connects to a detector and its output connects to a recorder. The detector has an output impedance of  $5\text{k}\Omega$ , and produces a voltage signal of  $1.2 \sin(\omega t)$  mV without any load (i.e., without connecting to the amplifier). The recorder has an input impedance of  $50\Omega$ . What is the signal received by the recorder?
6. (10 points) The drain-source voltage  $V_{DS}$  and drain current  $I_D$  of JFETs has the following typical relationship:  $I_D = I_{D(\text{sat})}(1 - e^{-V_{DS}/V_0})$ , where  $I_{D(\text{sat})} = I_{DSS}[1 - (V_{GS}/V_{GS(\text{off})})]^2$ . A given JFET, which is used as a voltage-controlled variable resistor shown in Figure 4, has  $V_0 = 5\text{V}$ ,  $I_{DSS} = 100\text{mA}$ , and  $V_{GS(\text{off})} = -5\text{V}$ . Define the resistance of the variable resistor as  $R_V$ . Under the condition of  $V_{DS} \ll 5\text{V}$ , what are the values of  $R_V$  at  $V_{GS} = -4\text{V}$  and  $V_{GS} = 0$ ?
7. (10 points) Refer to Figure 5. Which mode (depletion, enhancement, or neither) is each D-MOSFET biased? In each circuit, what are the sign (positive or negative) of  $V_{GS}$  and the direction (flowing into or out of the drain) of  $I_D$ ?
8. (Total 16 points) [a] (8 points) 請以元件的構造圖與電荷分佈，說明  $p$ -channel JFET 的如何以電壓控制電流的原理，要標示電壓的正或負極性及電荷是電子或電洞。[b] (8 points) 請以元件的構

造圖與電荷分佈，說明 *p*-channel E-MOSFET 如何以電壓控制電流的原理，要標示電壓的正或負極性及電荷是電子或電洞。

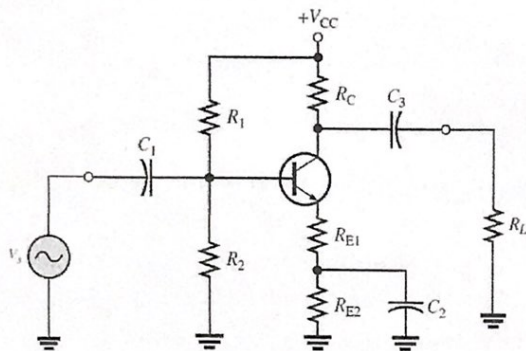


Figure 1

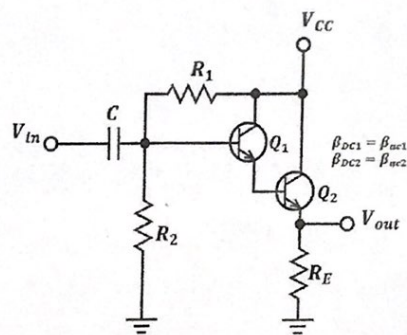


Figure 2

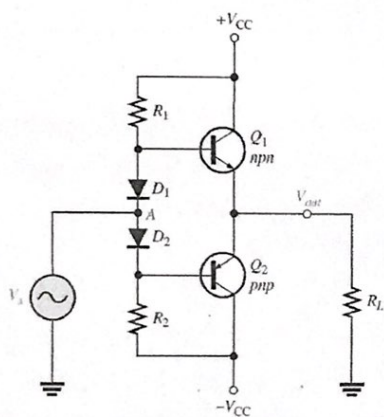


Figure 3

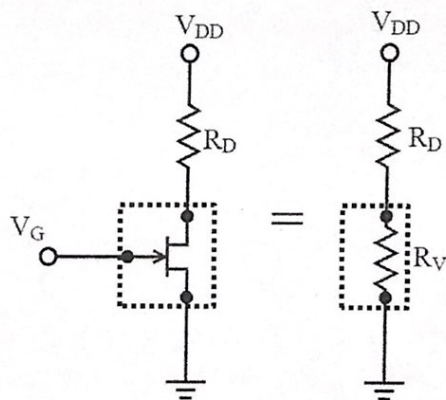


Figure 4

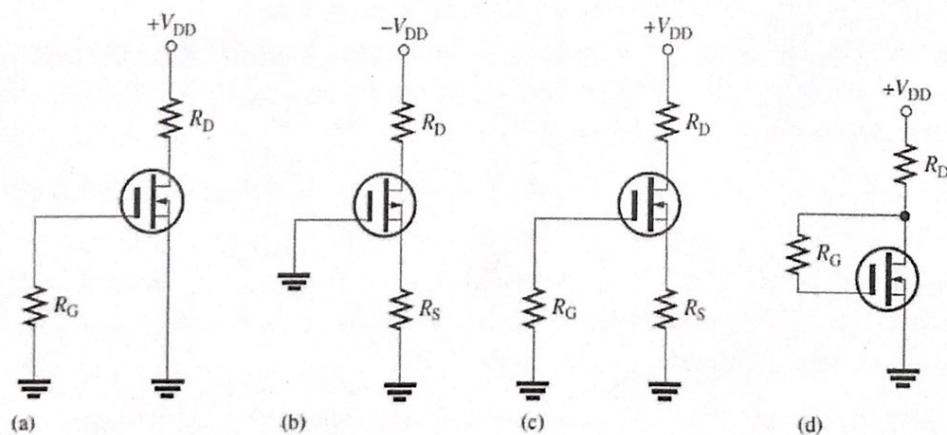


Figure 5